



INDIAN INSTITUTE OF INFORMATION  
TECHNOLOGY, NAGPUR

---

**CMOS  
Design(ECL-  
312)**

**Project  
Report**

---

*Submitted By :*

Rushikesh marade

(BT20ECE097)

Semester 6

Electronics and Communication Engineering  
Dept.

*Submitted To :*

Dr. Paritosh D. Peshwe

Course Instructor

# Contents


1. Aim
2. Theory
3. Implement full adder using transmission gate by writing netlist in NGSPICE
  - a. Circuit Diagram
  - b. Netlist
  - c. Output of netlist
4. Draw the layout of full adder using transmission gate in MicroWind
  - a. Layout Design
  - b. Output of Layout Design
5. Implement transmission gate based adiabatic full adder in NGSPICE
  - a. Circuit Diagram
  - b. Netlist
  - c. Output of netlist
6. Draw the layout of transmission gate based adiabatic full adder
  - a. Layout Design
  - b. Output of Layout Design
7. Conclusion

# Aim

Perform the following operations

1. Implement full adder using transmission gate by writing netlist in NGSPICE.
2. Draw the layout of full adder using transmission gate in MicroWind.
3. Implement transmission gate based adiabatic full adder in NGSPICE.
4. Draw the layout of transmission gate based adiabatic full adder

# Theory

 

A,B,C are inputs

S is sum

Co is carry output

\* Boolean Expression-

For Sum-

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$S = ABC + \bar{C}(A + B + C)$$

For Carry out-



$$Co = AB + BC + AC$$

$$Co = AB + C(A + B)$$

- Transmission gate based Full adder-

Carry generate(G)=A.B

- Carry Propagate(p)=A+B /  $A \oplus B$

  

- Transmission based Adder Expression:-

SUM-

$$S = ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$S = C(AB + \bar{A}\bar{B}) + C(A\bar{B} + \bar{A}B)$$

$$S = C(A \odot B) + C(A \oplus B)$$

$$\text{Let } x = A \oplus B$$

$$x = A \odot B$$

$$S = C \cdot x \oplus C \cdot x$$

$$= x \oplus C$$

$$S = A \oplus B \oplus C$$

$$S = P \oplus C$$

$$[P = A \oplus B]$$

Carry out-

$$Co = AB + BC + AC$$



$$Co = AB + C(A+B)$$

$$Co = G + PC$$

$$= A.B + PC$$

$$Co = AP + PC$$

- Design-

  

- Comparing above design and expression I make the circuit diagram and layout

- Truth Table-

A	B	C	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Implement full adder using transmission gate by writing netlist in NgSpice

# Circuit

Above is the circuit diagram of full adder using transmission gate logic. The detailed node numbering is also shown which is used in writing its netlist.

# Netlist-

```
**Full Adder using transmsion gate
.subckt inverter 1 2 3
mp 2 1 3 3 pmod w=100u l=10u
mn 2 1 0 0 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends

.subckt trans and 1 2 3 4
mp 4 3 1 1 pmod w=100u l=10u
mn 4 2 1 1 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends

Vdd 1 0 dc 5V
Va 11 0 pulse(0 5 0 0 0 10ms 20ms)
Vb 12 0 pulse(0 5 0 0 0 20ms 40ms)
Vc 13 0 pulse(0 5 0 0 0 40ms 80ms)
xa 11 14 1 inverter
xb 12 15 1 inverter
xc 13 16 1 inverter
xa and b' 11 15 12 17 trans and
xb and a' 14 12 15 17 trans and
xy 17 18 1 inverter
xc and y' 13 18 17 19 trans and
xy and c' 16 17 18 19 trans and
xc and y 13 17 18 20 trans and
xa and y' 11 18 17 20 trans and
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.tran 0.01ms 200ms
.control
run
```



```
plot V(11) V(12) V(13)
plot V(19) V(20)
.endc
.end
```
  
## # Output of Netlist-

The node numbering and their corresponding variables are indicated below:


- $V(11) \rightarrow A$
- $V(12) \rightarrow B$
- $V(13) \rightarrow C$
- $V(19) \rightarrow \text{Sum}$
- $V(20) \rightarrow \text{Carry}$






#Draw the layout of full adder using transmission gate in MicroWind-

\*Layout Design-

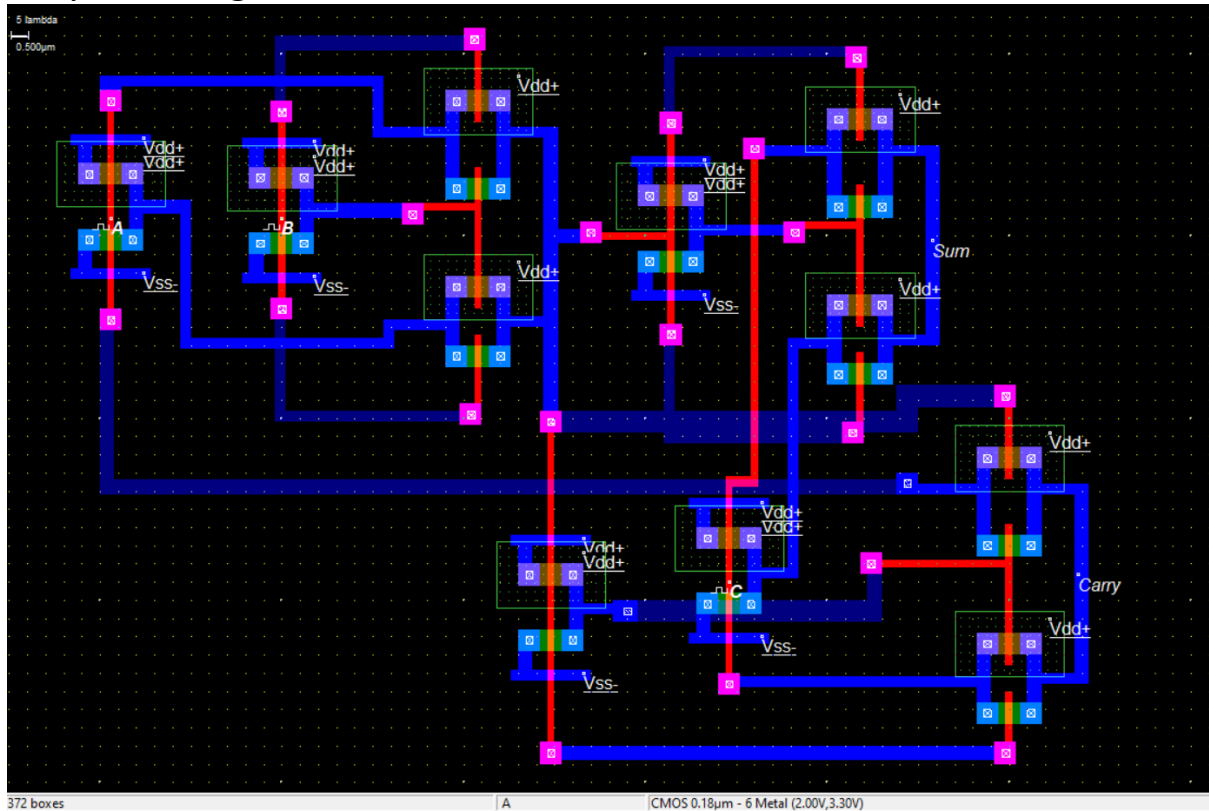

- Output of Layout Design-

 

We have used 6 transmission gates for constructing a full adder. The layout of the same has been shown above along with its result. The output graph shown some intermediate values since we have used transmission gate for its construction. The power dissipated by the full adder using transmission gate is  $52.823\mu\text{W}$ .

This power can be reduced using the adiabatic circuits, i.e., adiabatic full adder using transmission gate.

- Implement transmission gate based adiabatic full adder in NgSpice
- Circuit Diagram-

Above are the circuit diagrams of adiabatic full adder using transmission gate logic. First we have the normal full adder using transmission gate and the output of that adder is multiplied by a pulsating signal generated through A, B and C which is shown in the second circuit diagram above. The detailed node numbering is also shown which is used in writing its netlist.

- Netlist

**\*\*Adiabatic Full Adder using transmsion gate**

```
.subckt inverter 1 2 3
mp 2 1 3 3 pmod w=100u l=10u
mn 2 1 0 0 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends
```

```
.subckt trans and 1 2 3 4
mp 4 3 1 1 pmod w=100u l=10u
mn 4 2 1 1 nmod w=100u l=10u
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.ends
```

```
Vdd 1 0 dc 5V
Va 11 0 pulse(0 5 0 0 0 10ms 20ms)
Vb 12 0 pulse(0 5 0 0 0 20ms 40ms)
Vc 13 0 pulse(0 5 0 0 0 40ms 80ms)
xa 11 14 1 inverter
xb 12 15 1 inverter
xc 13 16 1 inverter
xa and b' 11 15 12 17 trans and
xb and a' 14 12 15 17 trans and
xy 17 18 1 inverter
xc and y' 13 18 17 19 trans and
xy and c' 16 17 18 19 trans and
xc and y 13 17 18 20 trans and
xa and y' 11 18 17 20 trans and
xa and a 11 11 14 21 trans and
```



```

xb    and b 12 12 15 21 trans and
xz    21 22 1 inverter
xz    and z 21 21 22 23 trans and
xc    and c 13 13 16 23 trans and
xp    23 24 1 inverter
xs    and p 19 23 24 25 trans and
xc    and p 20 23 24 26 trans and
.model nmod nmos level=54 version=4.7
.model pmod pmos level=54 version=4.7
.tran 0.01ms 200ms
.control
run
plot V(11) V(12) V(13)
plot V(25) V(26)
.endc
.end

```

  
## • Output of Netlist-

- V(11) → A
- V(12) → B
- V(13) → C
- V(25) → Sum of adiabatic circuit
- V(26) → Carry of adiabatic circuit




- Draw the layout of transmission gate based adiabatic full Adder

# layout Design-

 

## # Output of layout Design-

 

We have initially 6 transmission gate used for initial full adder and then additionally we have 4 extra transmission gate, in total we have 10 transmission gate used in adiabatic full adder using transmission gate logic.

We have given a pulsating signal through A, B and C, which has the expression of,  $V_{AC} = A + B + C$ .

By multiplying this  $V_{AC}$  to sum and carry of normal full adder we have reduced the power dissipation of the total circuit. The power dissipated came out to be  $0.103\mu W$ .

## • Conclusion-

We have got the same output wave forms for the normal full adder using transmission gate and the adiabatic full adder.

The power dissipation of adiabatic full adder using transmission gate is less than the normal full adder using transmission gate. We have reduced the power dissipation upto 48.56% using the adiabatic circuit.